

Sequential Circuits

Table of contents

Combinational vs sequential	1
State	2
General structure of a sequential circuit	2
Synchronous sequential circuits	2

A **sequential circuit** is a circuit whose output depends not only on the current inputs but also on the values it is currently storing. The storage is done with flip-flops — see flip-flops-and-latches¹ for the storage elements themselves.

Combinational vs sequential

	Combinational	Sequential
Contents	Logic gates only (no flip-flops)	Includes flip-flops as well as logic gates
Output determined by	The inputs alone — uniquely	Current inputs and current state
Repeatability	Same inputs always give the same output	Same inputs can give different outputs, depending on state
When output changes	Whenever an input changes	Only when the clock ‘ticks’
Examples	Adders, multiplexers, decoders, demultiplexers, encoders (see combinational-logic-blocks ²)	Counters, registers (see counters ³ , shift-registers ⁴)

¹courses/csse2010/flip-flops-and-latches.pdf

²courses/csse2010/combinational-logic-blocks.pdf

³courses/csse2010/counters.pdf

⁴courses/csse2010/shift-registers.pdf

A combinational example from earlier in the course: A into one input of an AND gate, B and C into an OR gate whose output feeds the AND gate's other input, giving $X = A(B + C)$. Nothing in that circuit remembers anything — change A , B or C and the output follows immediately (after propagation delay; see timing-diagrams⁵).

The key contrast: if an input to a combinational circuit changes, the output can change too and the **previous value is lost forever**. A sequential circuit can hold onto a value even after the input that produced it has gone away.

State

- **State** = the value stored in the flip-flops.
- **Output** depends on the inputs *and* the state.
- **Next state** depends on the inputs *and* the (present) state.

“Present state” is what the flip-flops hold right now; “next state” is what they will hold after the next clock edge. The combinational logic computes the next state from the present state and the inputs; the flip-flops only adopt it when the clock edge arrives.

General structure of a sequential circuit

The standard block diagram has two blocks and a feedback loop:

- A **combinational circuit** block (just logic gates). It takes the external **inputs** *plus* the feedback from the flip-flops, and produces the external **outputs** *plus* the values to be loaded into the flip-flops.
- A **flip-flops** block (the storage elements). Its data inputs come from the combinational circuit; it also takes **clock pulses** as a separate control input.
- A **feedback path** runs from the flip-flops' outputs back around into the combinational circuit's inputs. That loop is what makes the circuit sequential — the stored state is fed back in and influences the next output and the next state.

Note that the clock pulses go **only** to the flip-flops, not to the combinational logic.

Synchronous sequential circuits

In a **synchronous** sequential circuit the storage elements can only change at **discrete instants of time**, set by a common clock signal:

- Assume a clock signal — a regularly repeating square wave alternating between 0 and 1.
- The outputs of the storage elements change **only on the edges** of that control signal.

⁵[courses/csse2010/timing-diagrams.pdf](https://courses.csse2010/timing-diagrams.pdf)

- Contrast with logic gates, whose outputs change whenever their inputs change.

Because every flip-flop shares the same clock, the whole circuit's state changes in one step at each clock edge, which is what makes such circuits tractable to design and analyse.